

Bipolar analog output voltage

The op-amp and two resistors convert the difference $(I_{out} - \bar{I}_{out})$ into a voltage V_o .

$$V_o = (I_{out} - \bar{I}_{out}) R_F$$

I_{out} drives V_o positive while \bar{I}_{out} drives it negative. If D increases by one bit, I_{out} increases by one bit while \bar{I}_{out} decreases by one bit. \therefore The difference $(I_{out} - \bar{I}_{out})$ increases by two bits. \therefore The bipolar output voltage span is twice that of unipolar case.

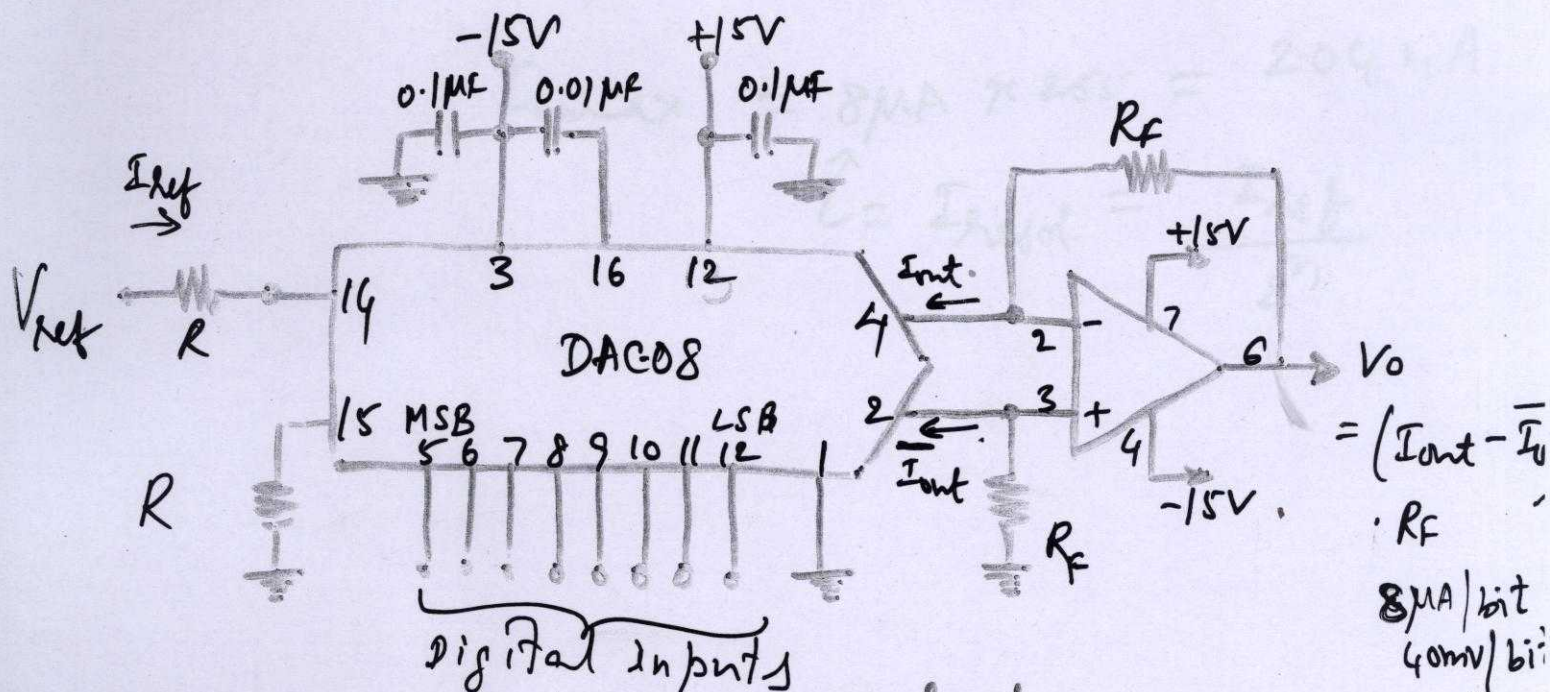


Fig. DAC-0808 connected for bipolar output voltage

$$V_o = (I_{out} - \bar{I}_{out}) R_F$$

$$= I_{res} [D - (255 - D)] \times R_F = I_{res} \cdot R_F (2D - 255)$$

8 μA /bit
40mV/bit
with
 $V_{ref} = 10.24$
&
 $R = 51$
 $= R_1$

Bipolar conversion (DAC)

	Digital inputs								Analog outputs	
	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	I _{int} (mA)	V _o (V)
Negative full scale	0	0	0	0	0	0	0	0	0	-10.2
Negative zero	0	1	1	1	1	1	1	1	1.016	-0.04
Positive zero	1	0	0	0	0	0	0	0	1.024	0.04
Positive full scale	1	1	1	1	1	1	1	1	2.040	10.2

Corresponding \bar{I}_{int} (mA):

2.04
1.024
1.016
0.0

$$I_{max} = 8mA \times 255 = 2.04 mA$$

$$\hat{I} = I_{resol.} = \frac{I_{ref}}{2^n}$$