

National Institute of Technology, Tiruchirappalli  
E. E. E. Department

# ***OPERATIONAL AMPLIFIERS***

# Introduction to Operational Amplifiers

- ‘Integrated Circuit’ is a multi-component circuit in which all the components are fabricated on the same chip
- ‘Integrating’ is a process of fabricating a single device which functions as a multi-component circuit

## **Advantages** of integration

- Miniaturisation
- Superior performance (better than discrete component circuits)
- Economical (when ?)
- Long and trouble-free operation

## **Disadvantages?**

Types of ICs: a) Linear ICs and b) Digital ICs

### **Linear ICs:**

- Equivalents of discrete transistor networks such as amplifiers, filters, modulators, frequency multipliers etc.
- Often require additional components for satisfactory operation.
- Output signals vary in proportion to the input signal (s). Signals are analogous to physical quantities (**Analog ICs**).


### **Digital ICs:**

- These are complete, functioning logic circuits such as gates, counters, flip-flops etc.
- Only a power supply and input signal are required. Primarily concerned with High or Low logic voltage levels
- Easy to design since accuracy is not required

## **The Operational Amplifier**

- Op-Amp is the most fundamental of the Linear ICs.
- Is a direct coupled high gain amplifier
- Most widely used linear IC – versatile amplifier
- Historically been the great grand-parent of computers
- OP-Amp  $\mu A741$  Introduced for first time in 1968 by Fairchild company


# OP-AMP 741 IC

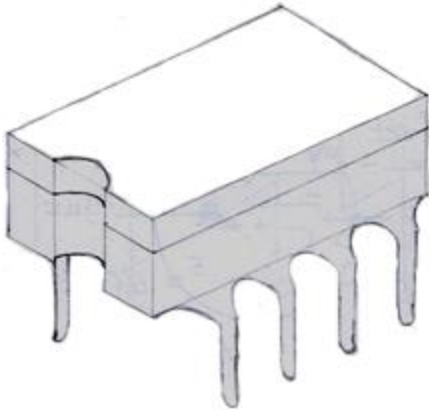


Plastic DIP



Metal Can Package (MCP)

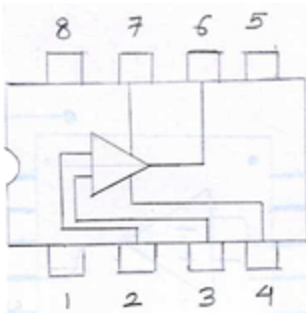


Top view of DIP

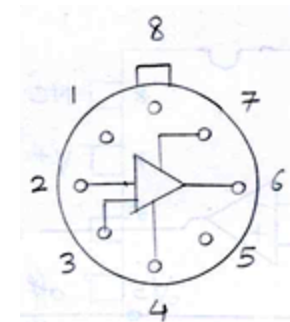


Top view of MCP

# Circuit symbol

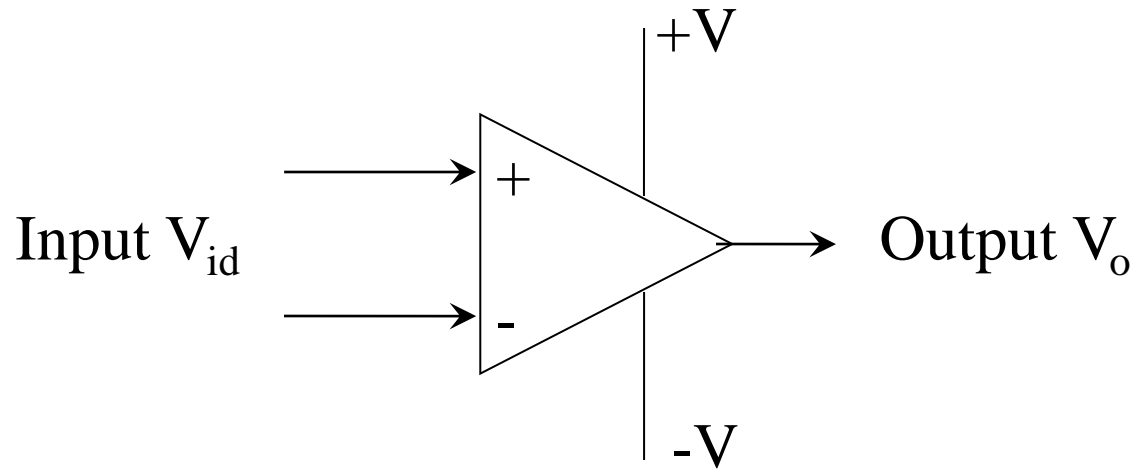

$$\text{Output } V_o = AV_{id}$$

## THE INSIDE STORY

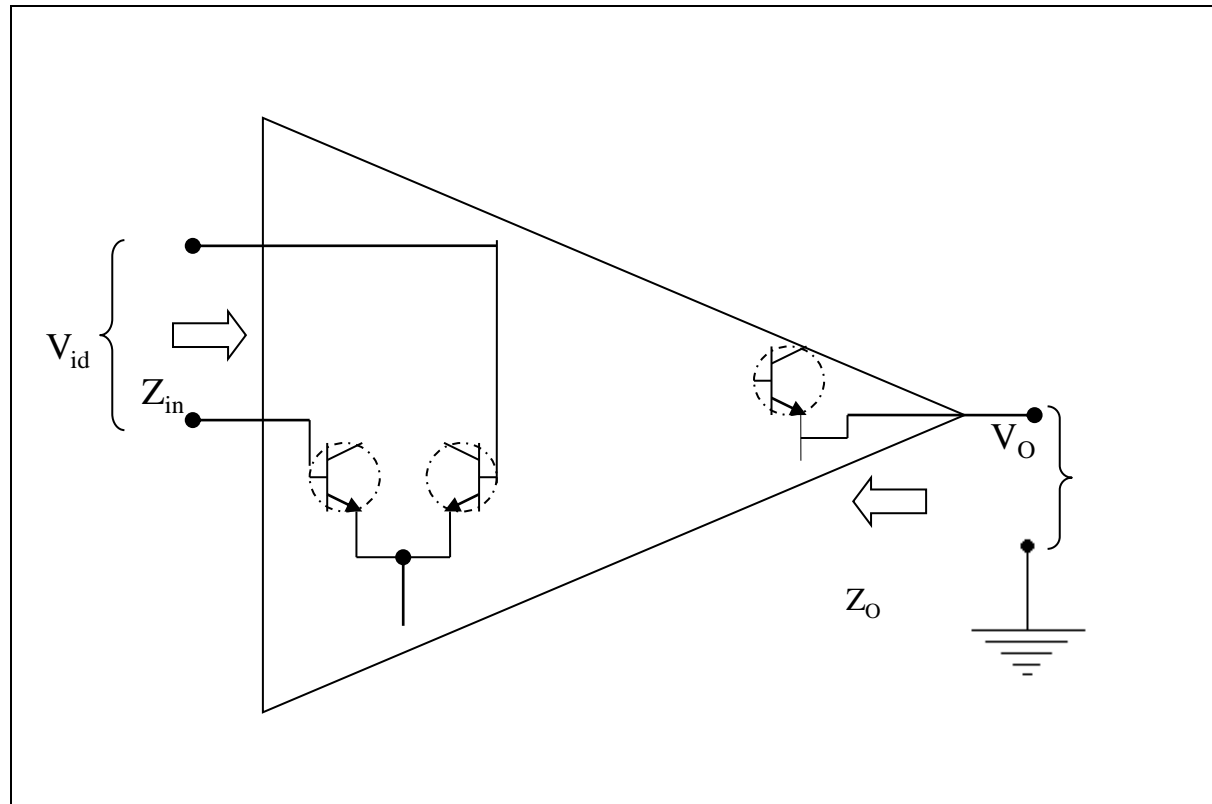


Differential Amplifier Input Stage and Emitter Follower Output Stage

## Characteristics of an ideal op-amp

1. Infinite voltage gain  $A$  in open loop
2. Infinite input resistance  $R_i$  – no loading
3. Zero output resistance  $R_o$  – can drive a no. of loads
4. Infinite bandwidth – no attenuation or distortion to ' $\infty$ ' Hz
5. Infinite common mode rejection ratio
6. Zero output voltage when input voltage is zero
7. Infinite slew rate -- output changes simultaneously with the input



# Low frequency equivalent ckt

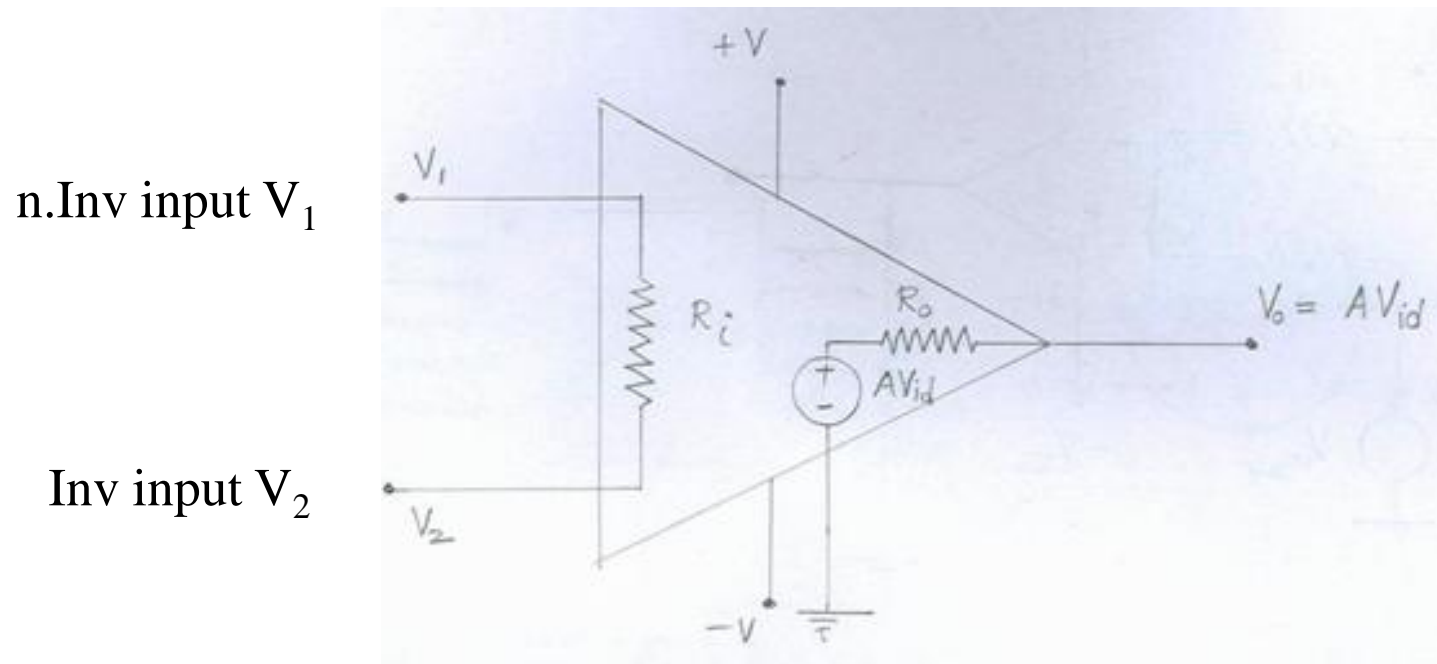

$$\text{Output } V_o = AV_{id} - i_o R_o = A(V_1 - V_2) - i_o R_o$$


Where  $A$  = large signal voltage gain.

$V_{id}$  = differential input voltage.

$V_1$  = voltage at n.inv. input terminal (w.r.t ground)


$V_2$  = voltage at inv. Input terminal (w.r.t ground)

# Operational model of OP-Amp

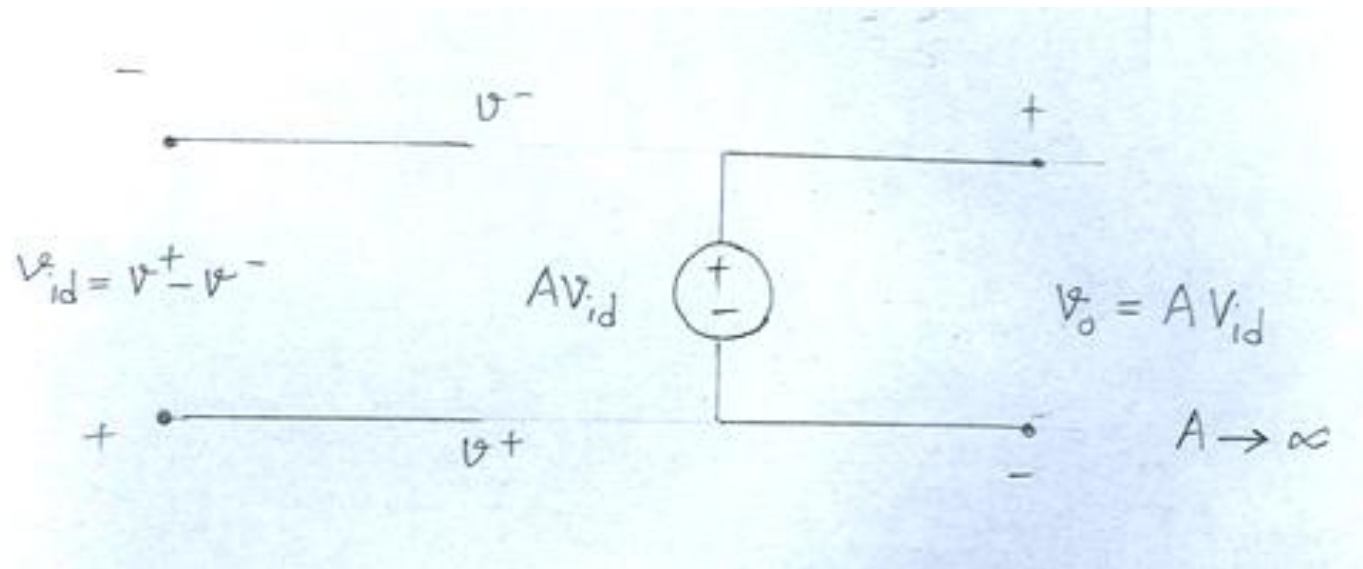
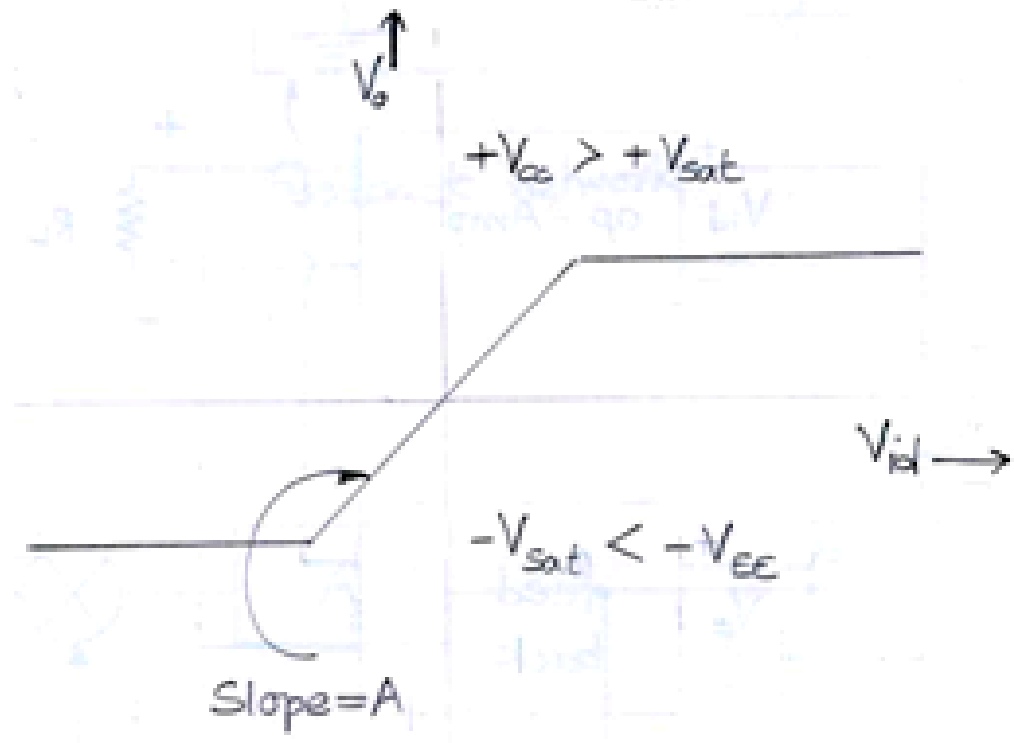
# Open-loop Voltage Transfer Characteristics

Maximum possible output voltage is governed by  $+V_{cc}$  &  $-V_{ee}$ .  
 $+V_{sat}$  &  $-V_{sat}$  are slightly less than  $+V_{cc}$  &  $-V_{ee}$  respectively.



# Closed loop configurations of Op-Amp

## **Disadvantages of open loop operation of Op-Amp**

- Clipping of output signal due to saturation
- Practically negligible operating range of input voltages ( $\mu\text{V}$ ) due to very high open loop gain
- Susceptible to noise
- Open loop gain not constant, affected by changes in temperature, power supply and production techniques
- The open loop bandwidth almost zero for the Op-Amp – unsuitable for ac applications
- Very limited applications such as a comparator

# **Advantages of closed loop operation of Op-Amp**

- Controllable gain using negative feedback of output – degenerative feedback
- Positive or regenerative feedback - used in oscillator circuits
- Increased bandwidth with negative feedback– suitable for ac applications
- Can further increase the input resistance and decrease output resistance
- Noise immunity and stability

# The golden rules for op-Amp circuits

## virtual ground concept

- When operated with negative feedback, an ideal op-Amp will do whatever it takes to drive  $v_{id}$  to zero. That is, it will force  $v_-$  to track  $v_+$  but without drawing any input current. Hence  $v_-$  tracks  $v_+$
- the input port looks like an open circuit for current (currents into op-Amp are zero)
- The input port looks like a short circuit for voltage ( $v_{id}$  is zero –**virtual short**)
- Due to very large open loop gain, the closed loop gain is independent of the open loop gain

# INVERTING AMPLIFIER

Inverting amplifier gain --

Assumptions: Infinite input impedance: hence  $i_1 = 0$ ;  $i_2 = 0$  and zero voltage drop between inputs i.e.,  $V_1 = V_2$ , and  $A = \infty$

Let  $R_s = 0$ , or include it as part of  $R_{in}$  ; then:  $i_{in} - i_f = 0$ ; i.e.,


$$\frac{V_{in} - 0}{R_{in}} - \frac{0 - V_{out}}{R_f} = 0$$

$$\text{closed loop gain} = \frac{V_{out}}{V_{in}}$$

Since  $A$  is very large 
$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

If  $A$  is not very large, then gain
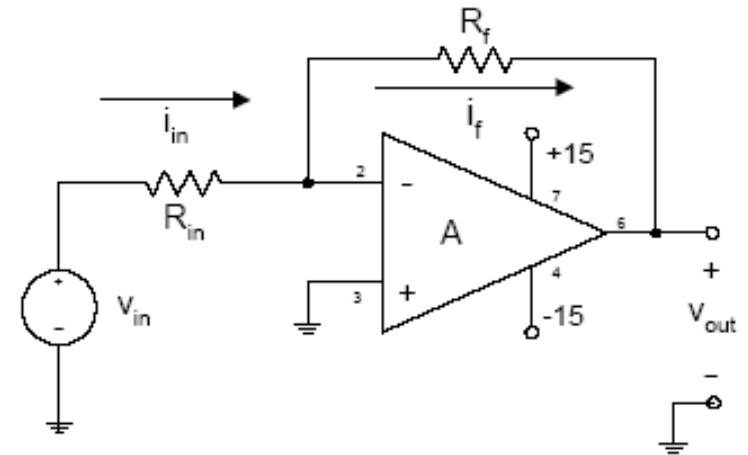
$$= -\frac{R_f}{R_{in}} \left[ \frac{1}{1 + (R_{in} + R_f) / AR_{in}} \right]$$





# NON-INVERTING AMPLIFIER


- Derivation of gain
- Assumptions: infinite input impedance: hence  $i_1 = 0$ ;  $i_2 = 0$ ; zero voltage drop between inputs i.e.,  $V_1 = V_2$  and  $A = \infty$ .

Since  $i_1 = 0$ ,  $V_1 = V_{in}$

Due to potential division,


$$V_2 = \frac{V_{out} R_1}{(R_1 + R_2)} = V_1 = V_{in}$$
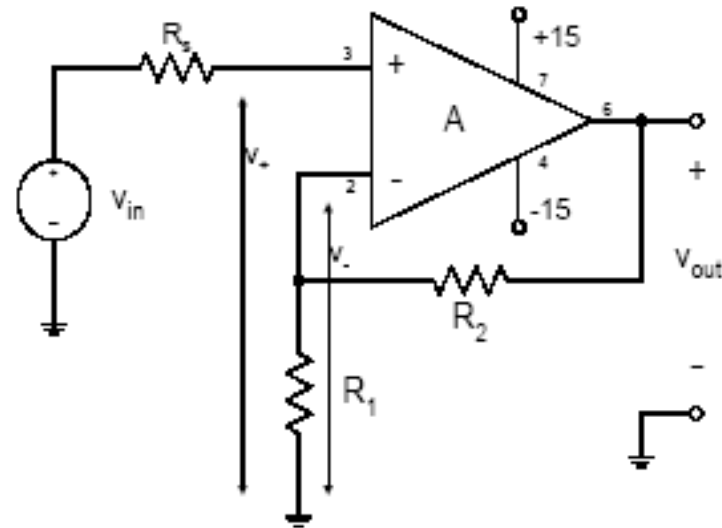
$$\text{hence } \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1}$$



# SUMMING AMPLIFIER (INVERTING)

## Summing amplifier

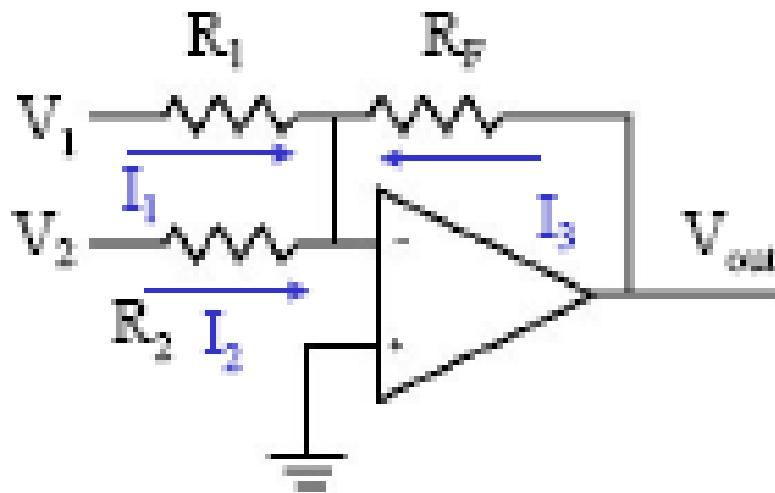


$$I_2 = -(I_1 + I_3)$$

$$\frac{V_2}{R_2} = -\left(\frac{V_1}{R_1} + \frac{V_{out}}{R_F}\right)$$

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\text{If } R_1 = R_2 = R_F, \text{ then } V_{out} = -(V_1 + V_2)$$
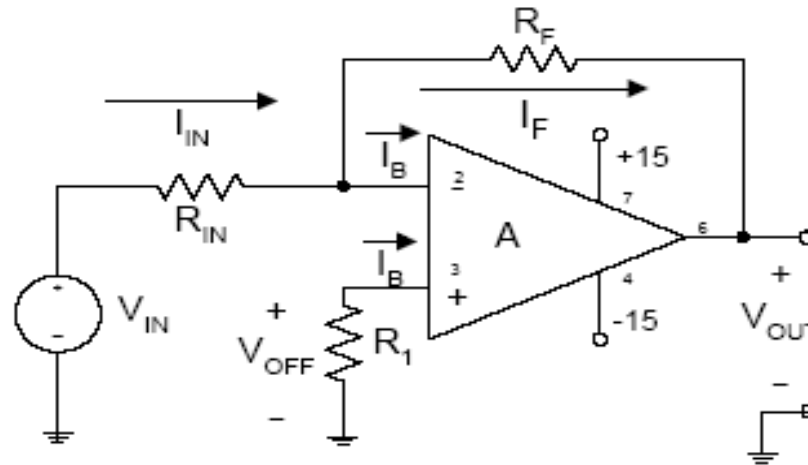
## INVERTING AMPLIFIER OFFSET DUE TO BIAS CURRENT



$$I_{IN} - I_B - I_F = 0$$

$$V_{OFF} = -R_1 I_B$$

$$\frac{V_{IN} - V_{OFF}}{R_{IN}} - I_B - \frac{V_{OFF} - V_{OUT}}{R_F} = 0$$

but with no input signal,  $V_{IN} = 0$ , and we want  $V_{OUT} = 0$ , so :

$$-I_B = V_{OFF} \left[ \frac{1}{R_{IN}} + \frac{1}{R_F} \right]; \quad -I_B = -R_1 I_B \left[ \frac{1}{R_{IN}} + \frac{1}{R_F} \right]$$

$$\text{thus : } \left[ \frac{1}{R_{IN}} + \frac{1}{R_F} \right] = \left[ \frac{1}{R_1} \right] \text{ as a condition for no offset at } V_o.$$

# Closed loop Difference amplifier

Use superposition theorem to analyze.

First consider  $V_y = 0$  (grounded)

So, with  $V_x$  alone, output is

$$V_{ox} = -V_x R_F / R_1 \quad \text{-----(1)}$$

With  $V_y$  alone (set  $V_x = 0$ )


$$V_{oy} = [(R_1 + R_F) / R_1] V_1$$

where  $V_1 = V_y [R_3 / (R_2 + R_3)]$

is the voltage at the non-inverting input terminal

Therefore
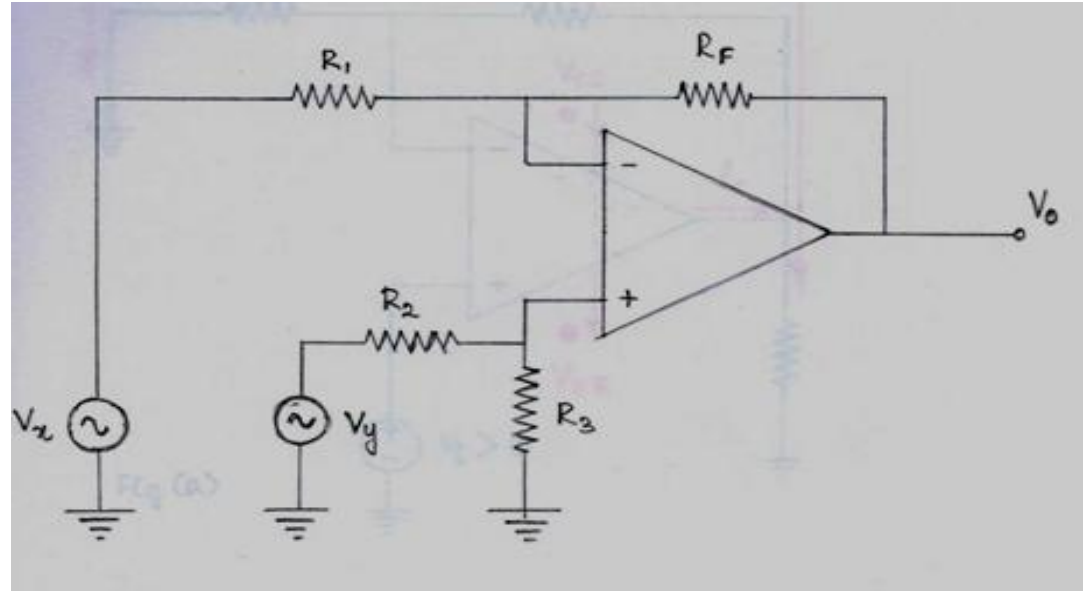
$$V_{oy} = [R_3 / (R_2 + R_3)] [(R_1 + R_F) / R_1] V_y \quad \text{-----(2)}$$



Summing (1) & (2) for total output  $V_o$  ,

$$\begin{aligned} V_o &= V_{ox} + V_{oy} \\ &= V_y \left[ \frac{R_3}{(R_2 + R_3)} \right] \left[ \frac{(R_1 + R_F)}{R_1} \right] - \left( \frac{R_F}{R_1} \right) V_x \quad \text{in general} \end{aligned}$$

If  $R_1 = R_2$  and  $R_3 = R_F$  , then

$$\begin{aligned} V_o &= V_y R_F / R_1 - V_x R_F / R_1 \\ &= R_F / R_1 (V_y - V_x) \\ &= -V_{xy} \cdot R_F / R_1 \quad (\text{similar to inv. Amp}) \end{aligned}$$