

Exercise – 6.2

Use **MATLAB (Simulink)** to

- i. simulate a three-phase controlled full wave rectifier supplying an R-L-E load for a given firing angle

Use **MATLAB Code** to

- ii. plot the variation of output voltage with respect to firing angle variation

Initial Calculations:

To construct the **6-pulse generator**:

- Phase delay (secs) in firing the thyristors of a three phase rectifier:

$$T_1 \rightarrow (30+\alpha)*10e-3/180$$

$$T_2 \rightarrow (90+\alpha)*10e-3/180$$

$$T_3 \rightarrow (150+\alpha)*10e-3/180$$

$$T_4 \rightarrow (210+\alpha)*10e-3/180$$


$$T_5 \rightarrow (270+\alpha)*10e-3/180$$

$$T_6 \rightarrow (330+\alpha)*10e-3/180$$

- Time period of pulses = 20 ms
- Pulse width (% of period) = 2 %


Simulink Circuit:

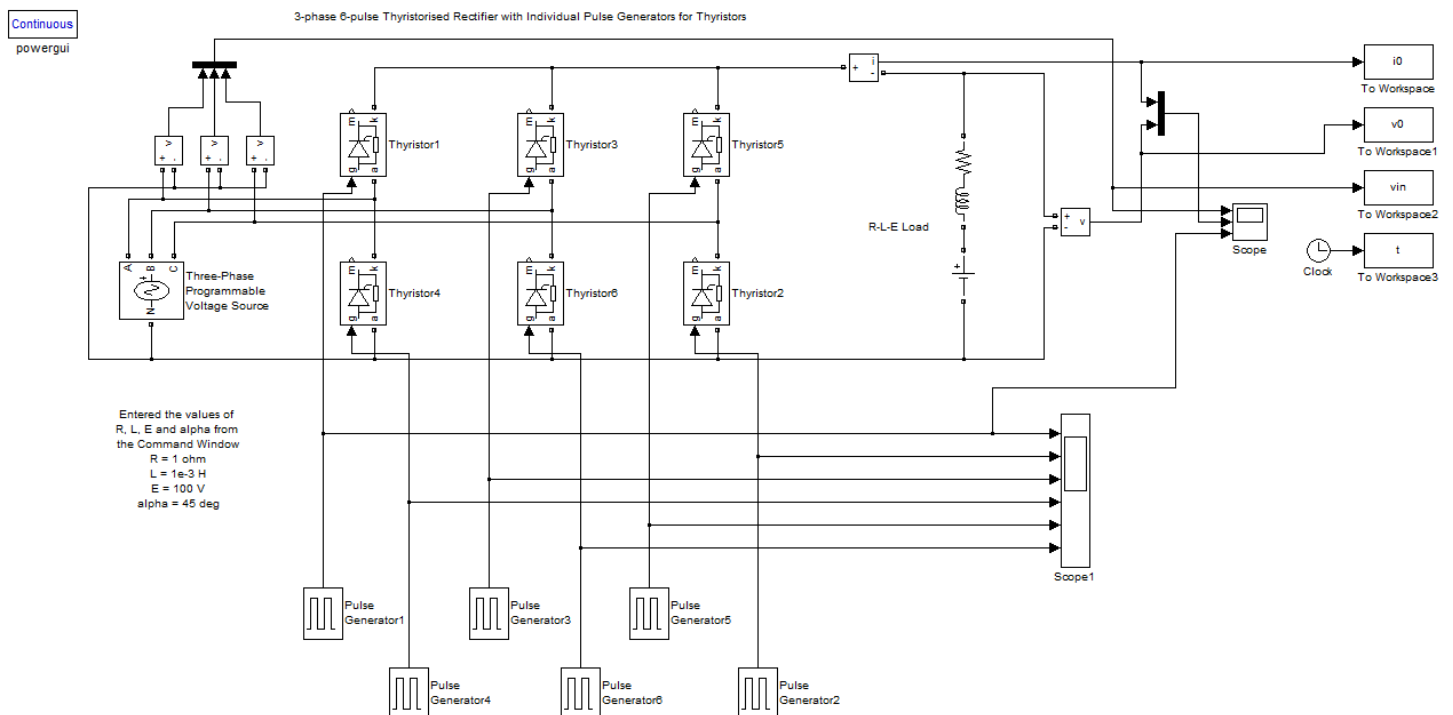i. Three-phase controlled full wave rectifier




Waveforms:

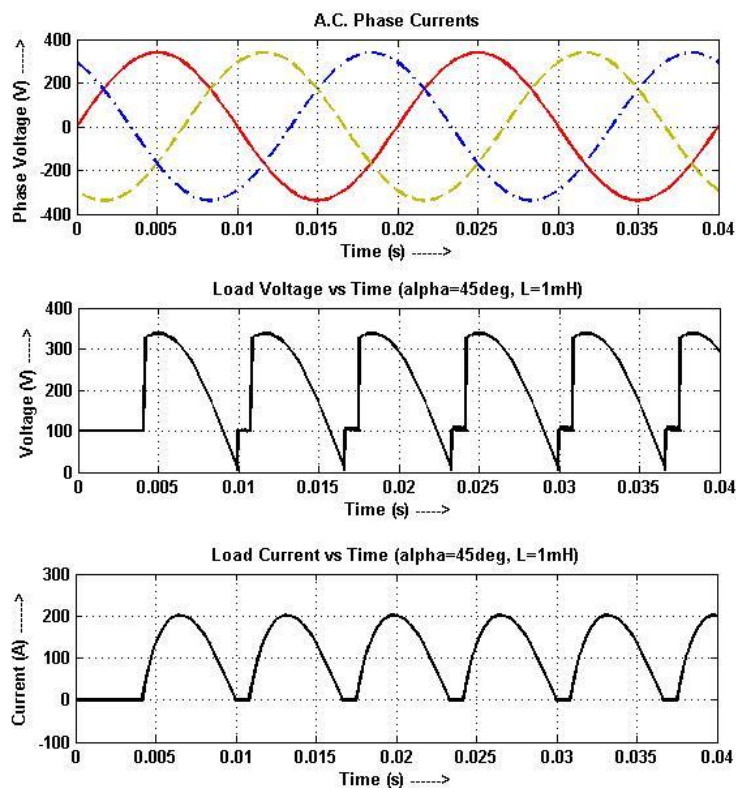1. Discontinuous Conduction Mode ($\alpha=45^\circ$, $L=1\text{ mH}$)



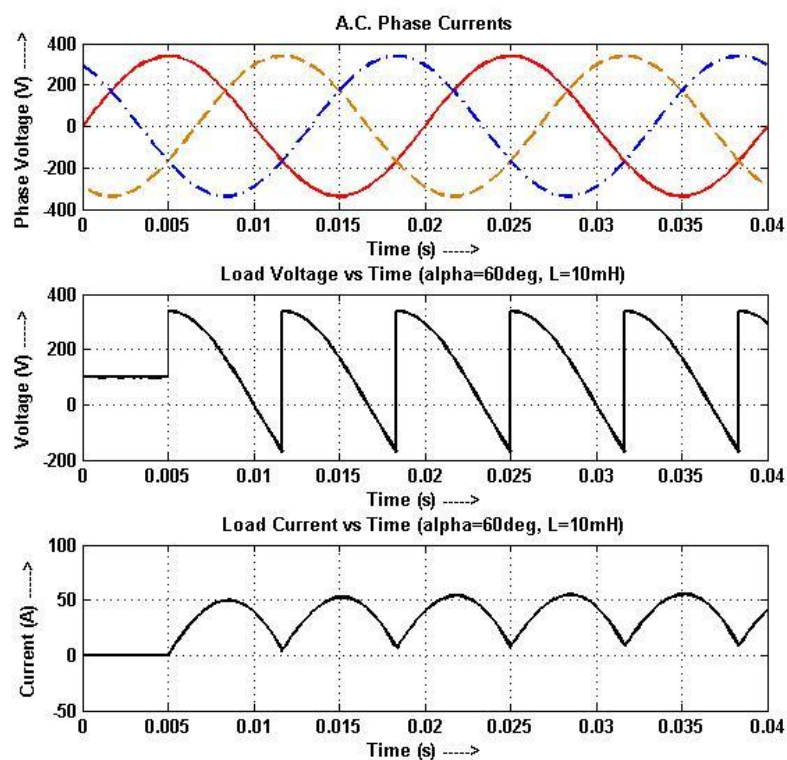2. Continuous Conduction Mode ($\alpha=60^\circ$, $L=10\text{ mH}$)



Formulae:

$$V_0 = \frac{3\sqrt{3}V_m}{\pi} \cos(\alpha)$$

m-code:


```
% Ex-6.2 (Power Electronics)
% Sambhav R Jain
% 107108103

clc;
clear all;
close all;

V = input('Enter the rms phase voltage: ');
Vm = V*sqrt(2);
alpha=0:0.01:180;
Vo=3*sqrt(3)*Vm/pi*cosd(alpha);
plot(alpha,Vo)
grid on
xlabel('Firing Angle (deg) ----->');
ylabel('Output Voltage (V) ----->');
title('Output voltage vs firing angle');
```

Plot:

(Phase Voltage rms, V=239.6 V)

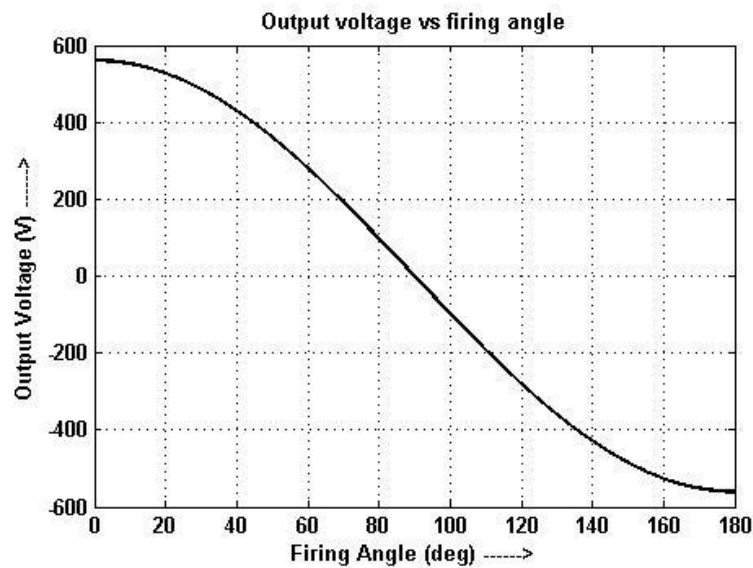

Results:

Hence the circuit of a three-phase controlled full wave rectifier supplying an R-L-E load is simulated using MATLAB-Simulink and the necessary waveforms are plotted for particular firing angles. Also, the variation of output voltage with varying firing angles is plotted with the help of MATLAB-Code.