

## EXPERIMENT #6

## COUNTERS

### I OBJECTIVES

The overall objective of this experiment is to familiarize students to design, build and test simple asynchronous counters using the TTL digital ICs.

### II COMPONENTS AND INSTRUMENTATION

Student's concentration should be on the TTL gates and flip flops. As well, you need a variety of resistors and LED's. For measurement, use a two channel oscilloscope with probes and a waveform generator. List of commonly available digital ICs and internal circuits are given at the end. The pin diagram and internal circuit of IC 7476 which is dual J-K flip-flop, is given below.

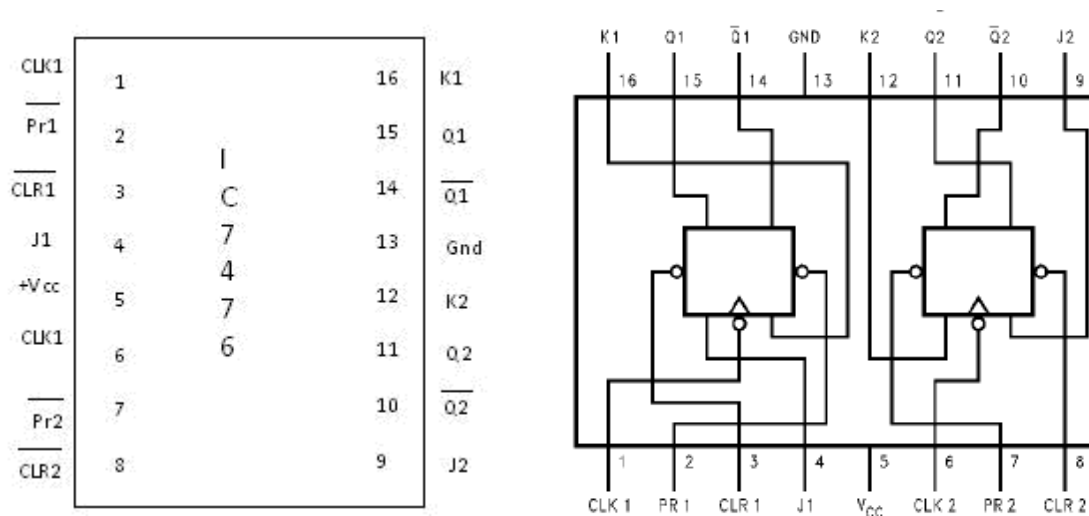


Fig. 6.1 Pin diagram and internal diagram of IC 7476 (dual J-K flip-flop)

### III PREPARATION

**P3.1** Connect the D input of the logic circuit shown in Fig. 6.2 to the pulse generator and set it at 1kHz. Connect the enable input (node E) to a logic high (+5V) through a 1k  $\Omega$  resistor. Observe the output; obtain the data for the Truth-table 6.1.

Then change the enable input to logic low. Leave the enable low and place a momentary short to ground first on Q and then on Q'. What happens to the output?

 


Fig. 6.2 Logic circuit

Table 6.1 Truth-table for Fig. 6.2

D	Q	Q'
0		
1		

### P3.2 - Asynchronous counters (optional question)

Asynchronous counters are a series of flip-flops each clocked by the previous state, one after the other. Since all the stages of the counter are not clocked together, a ripple effect propagates as various flip-flops are clocked. For this reason they are called ripple counters. The modulus of a counter is the number of different output states the counter may take (i.e. mod 4 means the counter has four output states).

In the pre-lab construct a 4-bit asynchronous counter shown in Fig.6.3. (It is also called binary ripple counter). Use four generic JK flip-flops. Connect four Binary Probes to Q outputs. Connect all R and S inputs to Logic 1 and connect a switch to the CP (clock pulse) input.

 



Fig. 6.3 4-bit asynchronous counter

Simulate the circuit using PSPICE or SEQUEL software and check that the output is as anticipated and print the waveforms and bring them to the lab.

## IV EXPLORATIONS

### E4.1

Use two 7476 ICs to implement the design of asynchronous counter to count up to 15 (as shown in Fig. 6.4). Connect the Q outputs of flip-flops to LEDs and connect all clear (CLR) and preset (PR) inputs to logic high.

 

**Table 6.2 Count Sequence for the 4-bit ripple counter**

---

---

*Integrated Circuits Lab manual*

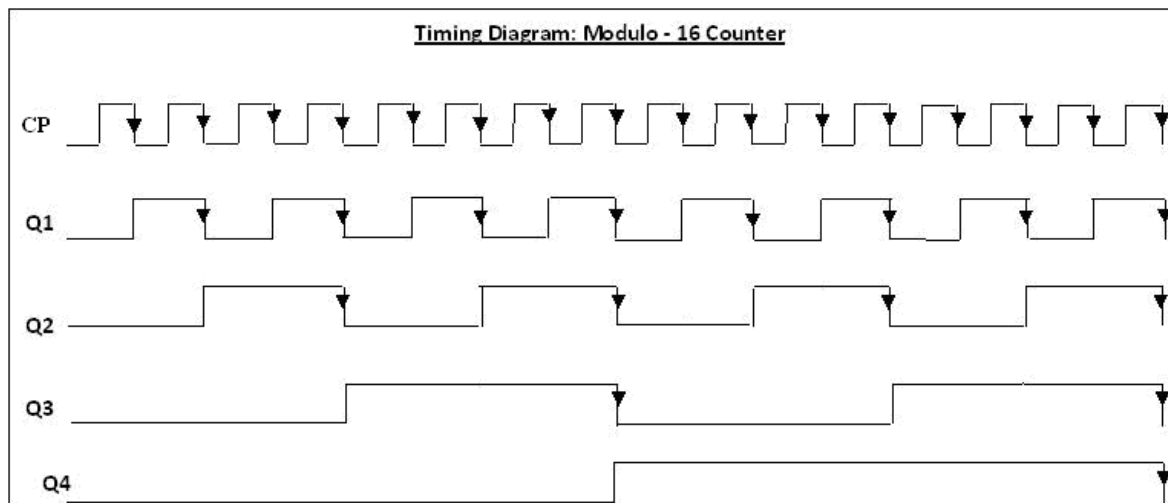


Fig.6.5 Timing sequence of input and output signals

#### E4.2 Mod-N counter

Design an asynchronous counter that goes through the count sequence \_\_\_\_\_.

How many flip-flops do you need? You may use any other gates for initiating 'Clear' operation. (choose from the pin details provided on page 6).

**Draw the circuit diagram.**

**Build and test the circuit. Demonstrate the counter operation.**

**Tabulate the counting sequence and draw the timing sequence waveforms on a graph sheet to be submitted in report.**

**Table 6.3 Count Sequence for the 4-bit ripple counter**

<b>Clock stage</b>	<b>Q1</b>	<b>Q2</b>	<b>Q3</b>	<b>Q4</b>

**V . INFERENCE / CONCLUSIONS**

 


Fig.6.6 Pin details of common digital ICs